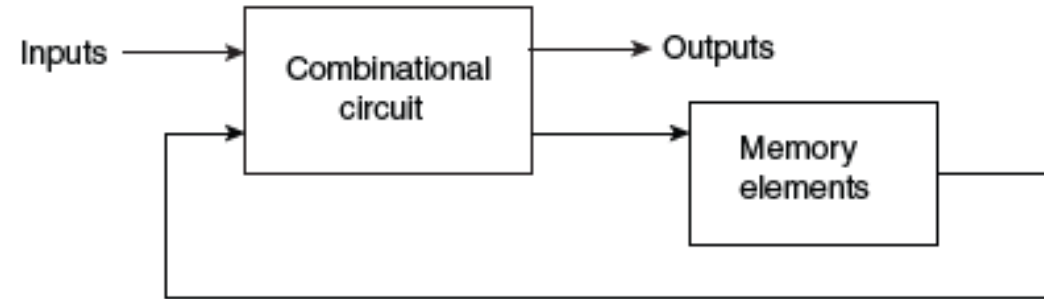


In this topic, we'll learn
Sequential Circuits

- Flip Flops
- State diagrams
- Counters

Introduction

- Sequential logic: Systems with combinational circuits and memory elements are described.
- Feedback path.
- Memory elements
 - Stores binary information
 - Binary information defines the state of the sequential circuit.
- External i/ps plus state of the memory elements determine the o/ps and the next state of the memory element.
- Sequential circuit is specified by a time sequence of i/ps, o/ps and internal states.



Synchronous vs Asynchronous Sequential Circuits (based on timing)

Synchronous

- Behavior can be defined from the knowledge of its signals at discrete instants of time.
- Synchronization by master-clock generator.
 - Produces periodic train of clock pulses.
 - Distributed throughout the system.
 - Memory systems are affected only with arrival of the synchronization pulse (AND gates)

Asynchronous

- Behavior depends upon
 - the order in which its i/p signals change
 - Can be affected at any instant of time.
- Memory devices used are time-delay devices.
- Unreliable due to variation in delays of the i/ps.

Clocked Sequential circuits



- Synchronous Sequential circuits that use clock pulses in the i/ps of the memory elements: Clocked Sequential circuits.
- Most frequent.
- Do not have instability problems.
- Timing is broken into independent discrete steps.
- Sequential circuits we discuss are clocked sequential circuits.
- Memory elements used are called flip-flops.
 - Binary cells capable of storing one bit of information.
 - 2 o/ps: normal and complement values.
 - Various types of flip-flops: based on the entry of binary information.

Flip-Flops

- Maintain a binary state indefinitely (as long as power is delivered to the circuit)
- States are switched when directed by i/p signals.
- Different types of FF
 - Number of i/ps
 - Manner in which i/ps affect the binary state.


Basic Flip-Flop circuit

  - Constructed from 2 NAND or NOR gates.
 - more complicated types can be built from these basic FFs.
- Cross-coupled connection from the o/p of one gate to the i/p of the other gate: Feedback
 - Asynchronous sequential circuits
- 2 o/ps: Q and Q' , 2 i/ps: set and reset
- Binary state of FF is the value of the normal o/p Q .



NOR Flip-Flop circuit

 
- Set: $S=1, R=0$
- Reset: $S=0, R=1$
- Memory: $S=R=0$
- Undefined: $S=R=1$



S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	

NAND Flip-Flop circuit


 
- Set: $S=0, R=1$
- Reset: $S=1, R=0$;
- Undefined: $S=R=0$
- Memory: $S=R=1$



S	R	Q	Q'	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	

Clocked *RS* Flip-Flop

  
- Graphic Symbol
 - triangle is a symbol for a *dynamic indicator*
 - Indicates: FF responds to an i/p clock transition from 0 to 1.
 - State of the FF is determined by Q .



Clocked *RS* Flip-Flop

- Characteristic table

Q	S	R	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

 

Clocked *RS* Flip-Flop


- Characteristic equation
 - specifies the value of the next state as a function of the present state and the inputs.
 - an algebraic expression for the binary information of the characteristic table.

		S			
		SR			
		00	01	11	10
Q	0			X	1
	1	1		X	1

$$Q(t + 1) = S + R'Q$$
$$SR = 0$$


Clocked *RS* Flip-Flop

 - Characteristic equation
 - specifies the value of the next state as a function of the present state and the inputs.
 - an algebraic expression for the binary information of the characteristic table.
 - two indeterminate states are marked by X 's.
 - $SR = 0$: both S and R cannot equal 1 simultaneously





D Flip-Flop (transfer “data”)

 - Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).



D Flip-Flop (transfer “data”)

  
- Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).
- Graphic Symbol



D Flip-Flop (transfer “data”)



- Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).
- Characteristic table

Q	D	$Q(t + 1)$
0	0	0
0	1	1
1	0	0
1	1	1

 



D Flip-Flop (transfer “data”)

  - Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).
- Characteristic Equation



JK Flip-Flop

  
- Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.



JK Flip-Flop

- Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.
- Characteristic Table

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


JK Flip-Flop

- Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.
- Characteristic equation


		J			
		JK		11	10
Q	0			1	1
	1	1			1
		K			
		00	01	11	10

$Q(t + 1) = JQ' + K'Q$

 

JK Flip-Flop

 - Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.
- If $CP=1$ and $J=K=1$
 - Repeated and continuous transitions of o/ps.
 - To avoid this
 - CP must be shorter than the propagation delay through the FF.





T Flip-Flop

- Single i/p version of JK FF.
 - Both J and K are tied together.
 - T stands for “toggle”, when $T=1$ and $CP=1$.
- Obtain the Characteristic Table and Characteristic equation.

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

			T
		0	1
Q	0		1
	1	1	
  
$$Q(t+1) = TQ' + T'Q$$


Different conventions used


Latch vs Flip-Flop

- Latch is level-triggered.
- Flip-Flop is edge-triggered.

Triggering of Flip-Flops

- Switch in the state of a FF by momentary change in the i/p signal
 - Momentary change: Trigger
- For Latches (Asynchronous FF) triggering is by change of signal level.
 - Level should return to its initial value (0 in NOR and 1 in NAND) before second trigger.
- Flip-Flops (Clocked FF) are triggered by pulses.
 - Pulse start from an initial value of 0, goes briefly to 1, and returns to its initial value of 0.
 - Time interval from the application of pulse until the o/p transition is **critical**.


Feedback path and instability

 

- Instability
 - If o/ps of FFs are changing while the o/ps of the combinational circuits (i/ps to FFs) are being sampled by the clock pulse.
- Can be prevented
 - If o/ps of FFs do not start changing until pulse i/p returns to 0.
 - Signal propagation delay of a FF from the i/p to o/p should be greater than the pulse duration. (Difficult to control)
 - Include a physical unit for the delay or
 - Make FF sensitive to pulse transition.

Definition of Clock pulse transition

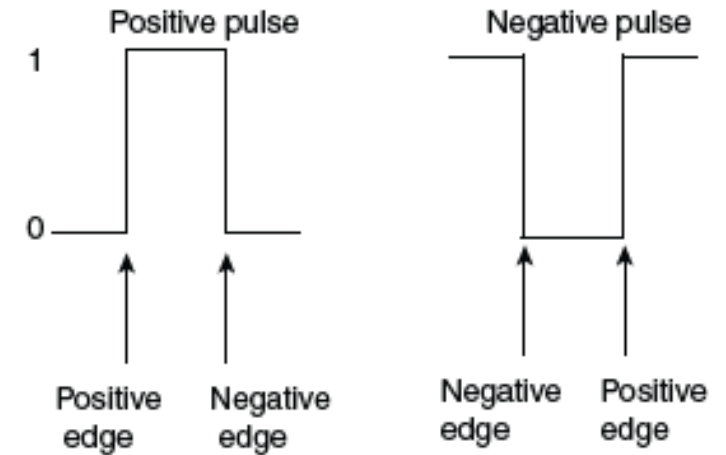- Positive pulse: 1 during the occurrence of pulse. 0 otherwise.
- 0 to 1: Positive edge
- 1 to 0 negative edge



Multiple-transition problem


- Clocked flip-flops introduced
 - Triggered during the positive edge of the pulse.
 - State transition starts immediately after pulse becomes 1.
 - New state of the FF may appear at the o/p while the pulse is still 1.
 - FF will start responding to these new values.
 - A new o/p may occur.
 - Hence, o/p of 1 FF cannot be applied to the i/p of another FF when both are triggered by the same clock pulse.
- Can be eliminated if FF respond to edge transition only.

Capacitive coupling

- RC circuit is inserted in the clock i/p of the FF.
 - Generates a spike in response to momentary change in i/p.
 - Positive spike: At positive Edge; Negative spike: At negative Edge
- Edge triggering: By designing the FF to respond to one spike and neglect the other.

Master-Slave Flip-Flop

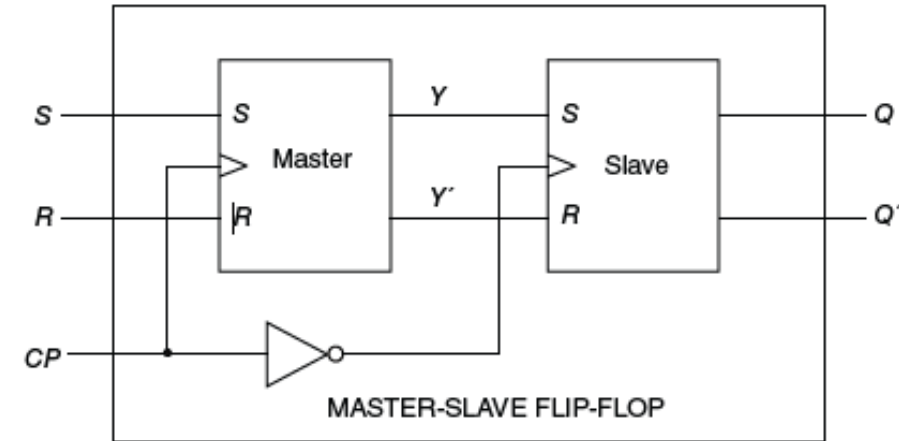
- Constructed from two separate FFs.
 - One master and other acts as slave.
- When $CP=0$
 - Slave is enabled.
 - $Q=Y$
 - Master is disabled.
- When $CP=1$
 - Master is enabled.
 - Information at S and R i/ps is transmitted to Y.
 - Slave is disabled.
-



- When CP returns to 0
 - Slave goes to the same state as the master.


Timing relationships in a master-slave flip-flop

 - Initially FF is cleared
 - $Y=Q=0$.
- S input can be changed at the same time that the pulse goes through its negative edge transition.
- Once the CP reaches 0, the master is disabled.
 - possible to use the same clock pulse to switch
 - output of the flip-flop
 - input information.
- State changes at the negative edge transition of the clock pulse.



Clocked master-slave JK flip-flop

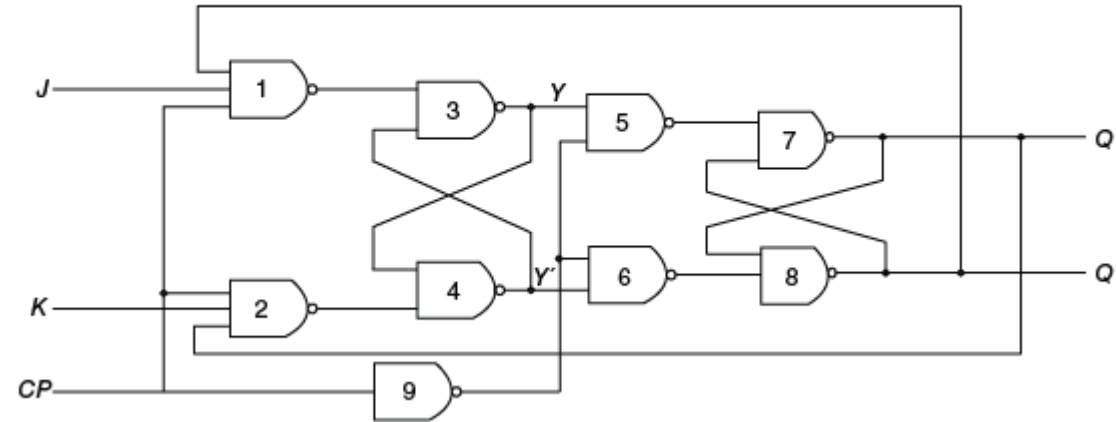- Gates 1 to 4: Master FF.
 - 5 to 8: Slave FF



Cascading of many Master-Slave FFs

- When pulse is 1 all the masters (internal to the FF) are enabled
 - O/p of the FFs are not affected.
- After the clock returns to 0.
 - Slaves are enabled.
 - O/ps of some of the FFs are changed.
 - None of the masters are affected by these changes.

Edge-Triggered Flip-Flop


- Output transitions occur at a specific level of the clock pulse
 - When the pulse input level exceeds this threshold level, i/ps are locked out.
 - Could be positive or negative edge triggered.

Design of Counters

- Counters: Sequential circuits which undergo **prescribed sequence of states** upon application of **i/p pulse**.
- I/p pulse: Called **count pulse**.
 - clock or from an external source.
 - Prescribed time or random.
- Sequence: binary (simplest and straightforward) or any other
- Used in all equipment with digital logic.
 - Number of occurrences.
 - Timing sequences to control operations.

Binary Counters

 - Simplest and straight forward.
- n-bit counter: **n FFs** and count from **0 to 2^n-1** .



- FF count **repeats**. Goes to 000 after 111.
- i/p and o/p values not shown.
- Clocked sequential circuits: State transitions during clock pulses. **Not shown** explicitly.
- Only i/p: **Count pulse**.
- O/ps: Specified by the **present states** of FFs.
- Next state
 - **Depends** only on the **present state**.
 - Transitions during clock pulses.
 - **Completely specified** by the count sequence.

Excitation Table for 3-bit counter

Table 6-12 Excitation table for a 3-bit binary counter

Count sequence			Flip-flop inputs		
A_2	A_1	A_0	TA_2	TA_1	TA_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	1	1	1

- **Next number** represents the **next state**.
- Count sequence:
Provides all information to design the circuit.
- Follows the **same procedure**.
- Excitation obtained **directly** from the count sequence.
- **Binary counters** most **effectively constructed** by T FFs.
- **Last row** compared with the first count **000**, its **next state**.

Review

- Flip-Flops
- Triggering of Flip-Flops
- Analysis of clocked sequential circuits
- State reduction and Assignment
- Flip-Flop Excitation Tables
- Conversion of one FF to another
- Design Procedure
- Design of counters
- Shift registers