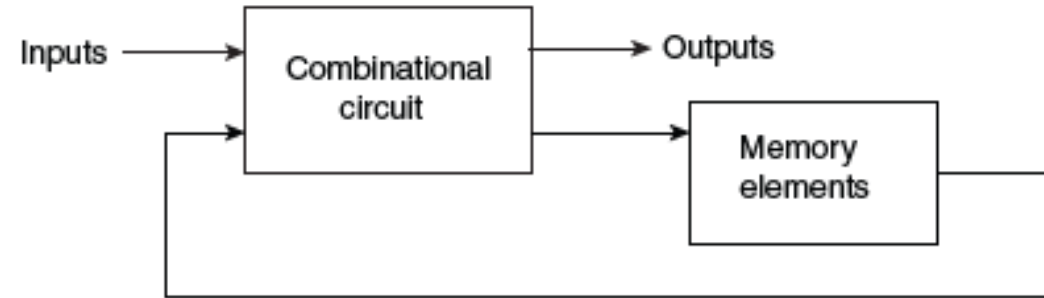


In this topic, we'll learn
Sequential Circuits

- Flip Flops
- State diagrams
- Counters

Introduction

- Sequential logic: Systems with combinational circuits and memory elements are described.
- Feedback path.
- Memory elements
 - Stores binary information
 - Binary information defines the state of the sequential circuit.
- External i/ps plus state of the memory elements determine the o/ps and the next state of the memory element.
- Sequential circuit is specified by a time sequence of i/ps, o/ps and internal states.



Synchronous vs Asynchronous Sequential Circuits (based on timing)

Synchronous

- Behavior can be defined from the knowledge of its signals at discrete instants of time.
- Synchronization by master-clock generator.
 - Produces periodic train of clock pulses.
 - Distributed throughout the system.
 - Memory systems are affected only with arrival of the synchronization pulse (AND gates)

Asynchronous

- Behavior depends upon
 - the order in which its i/p signals change
 - Can be affected at any instant of time.
- Memory devices used are time-delay devices.
- Unreliable due to variation in delays of the i/ps.

Clocked Sequential circuits



- Synchronous Sequential circuits that use clock pulses in the i/ps of the memory elements: Clocked Sequential circuits.
- Most frequent.
- Do not have instability problems.
- Timing is broken into independent discrete steps.
- Sequential circuits we discuss are clocked sequential circuits.
- Memory elements used are called flip-flops.
 - Binary cells capable of storing one bit of information.
 - 2 o/ps: normal and complement values.
 - Various types of flip-flops: based on the entry of binary information.

Flip-Flops

- Maintain a binary state indefinitely (as long as power is delivered to the circuit)
- States are switched when directed by i/p signals.
- Different types of FF
 - Number of i/ps
 - Manner in which i/ps affect the binary state.


Basic Flip-Flop circuit

  - Constructed from 2 NAND or NOR gates.
 - more complicated types can be built from these basic FFs.
- Cross-coupled connection from the o/p of one gate to the i/p of the other gate: Feedback
 - Asynchronous sequential circuits
- 2 o/ps: Q and Q' , 2 i/ps: set and reset
- Binary state of FF is the value of the normal o/p Q .



NOR Flip-Flop circuit

 
- Set: $S=1, R=0$
- Reset: $S=0, R=1$
- Memory: $S=R=0$
- Undefined: $S=R=1$



S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	

NAND Flip-Flop circuit


 
- Set: $S=0, R=1$
- Reset: $S=1, R=0$;
- Undefined: $S=R=0$
- Memory: $S=R=1$



S	R	Q	Q'	
1	0	0	1	
1	1	0	1	(after $S = 1, R = 0$)
0	1	1	0	
1	1	1	0	(after $S = 0, R = 1$)
0	0	1	1	

Clocked *RS* Flip-Flop

  
- Graphic Symbol
 - triangle is a symbol for a *dynamic indicator*
 - Indicates: FF responds to an i/p clock transition from 0 to 1.
 - State of the FF is determined by Q .



Clocked *RS* Flip-Flop

- Characteristic table

Q	S	R	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

 

Clocked *RS* Flip-Flop


- Characteristic equation
 - specifies the value of the next state as a function of the present state and the inputs.
 - an algebraic expression for the binary information of the characteristic table.

		S			
		SR			
		00	01	11	10
Q	0			X	1
	1	1		X	1

$$Q(t + 1) = S + R'Q$$
$$SR = 0$$


Clocked *RS* Flip-Flop

 - Characteristic equation
 - specifies the value of the next state as a function of the present state and the inputs.
 - an algebraic expression for the binary information of the characteristic table.
 - two indeterminate states are marked by X 's.
 - $SR = 0$: both S and R cannot equal 1 simultaneously





D Flip-Flop (transfer “data”)

 - Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).



D Flip-Flop (transfer “data”)

  
- Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).
- Graphic Symbol



D Flip-Flop (transfer “data”)



- Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).
- Characteristic table

Q	D	$Q(t + 1)$
0	0	0
0	1	1
1	0	0
1	1	1

 



D Flip-Flop (transfer “data”)

  - Modification of the clocked *RS* flip-flop
 - *RS* flip-flop with an inverter in the *R* input.
 - Also called *gated D-latch*.
 - *CP* input is often given the variable designation *G* (*for gate*).
- Characteristic Equation



JK Flip-Flop

  
- Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.



JK Flip-Flop

- Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.
- Characteristic Table

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


JK Flip-Flop

- Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.
- Characteristic equation


		J			
		JK		11	10
Q	0			1	1
	1	1			1
		K			
		00	01	11	10

$Q(t + 1) = JQ' + K'Q$

 

JK Flip-Flop

 - Refinement of the *RS* flip-flop
 - indeterminate state of the *RS* type is defined in JK.
- If $CP=1$ and $J=K=1$
 - Repeated and continuous transitions of o/ps.
 - To avoid this
 - CP must be shorter than the propagation delay through the FF.





T Flip-Flop

- Single i/p version of JK FF.
 - Both J and K are tied together.
 - T stands for “toggle”, when $T=1$ and $CP=1$.
- Obtain the Characteristic Table and Characteristic equation.

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

			T
		0	1
Q	0		1
	1	1	
  
$$Q(t+1) = TQ' + T'Q$$


Different conventions used


Latch vs Flip-Flop

- Latch is level-triggered.
- Flip-Flop is edge-triggered.

Triggering of Flip-Flops

- Switch in the state of a FF by momentary change in the i/p signal
 - Momentary change: Trigger
- For Latches (Asynchronous FF) triggering is by change of signal level.
 - Level should return to its initial value (0 in NOR and 1 in NAND) before second trigger.
- Flip-Flops (Clocked FF) are triggered by pulses.
 - Pulse start from an initial value of 0, goes briefly to 1, and returns to its initial value of 0.
 - Time interval from the application of pulse until the o/p transition is **critical**.


Feedback path and instability

 

- Instability
 - If o/ps of FFs are changing while the o/ps of the combinational circuits (i/ps to FFs) are being sampled by the clock pulse.
- Can be prevented
 - If o/ps of FFs do not start changing until pulse i/p returns to 0.
 - Signal propagation delay of a FF from the i/p to o/p should be greater than the pulse duration. (Difficult to control)
 - Include a physical unit for the delay or
 - Make FF sensitive to pulse transition.

Definition of Clock pulse transition

 - Positive pulse: 1 during the occurrence of pulse. 0 otherwise.
- 0 to 1: Positive edge
- 1 to 0 negative edge



Multiple-transition problem


- Clocked flip-flops introduced
 - Triggered during the positive edge of the pulse.
 - State transition starts immediately after pulse becomes 1.
 - New state of the FF may appear at the o/p while the pulse is still 1.
 - FF will start responding to these new values.
 - A new o/p may occur.
 - Hence, o/p of 1 FF cannot be applied to the i/p of another FF when both are triggered by the same clock pulse.
- Can be eliminated if FF respond to edge transition only.

Capacitive coupling

- RC circuit is inserted in the clock i/p of the FF.
 - Generates a spike in response to momentary change in i/p.
 - Positive spike: At positive Edge; Negative spike: At negative Edge
- Edge triggering: By designing the FF to respond to one spike and neglect the other.

Master-Slave Flip-Flop

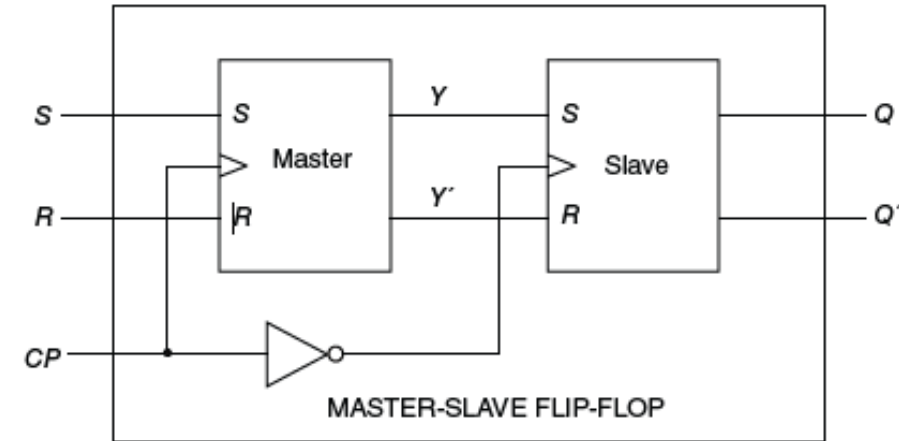
- Constructed from two separate FFs.
 - One master and other acts as slave.
- When $CP=0$
 - Slave is enabled.
 - $Q=Y$
 - Master is disabled.
- When $CP=1$
 - Master is enabled.
 - Information at S and R i/ps is transmitted to Y.
 - Slave is disabled.



- When CP returns to 0
 - Slave goes to the same state as the master.


Timing relationships in a master-slave flip-flop

 - Initially FF is cleared
 - $Y=Q=0$.
- S input can be changed at the same time that the pulse goes through its negative edge transition.
- Once the CP reaches 0, the master is disabled.
 - possible to use the same clock pulse to switch
 - output of the flip-flop
 - input information.
- State changes at the negative edge transition of the clock pulse.



Clocked master-slave JK flip-flop

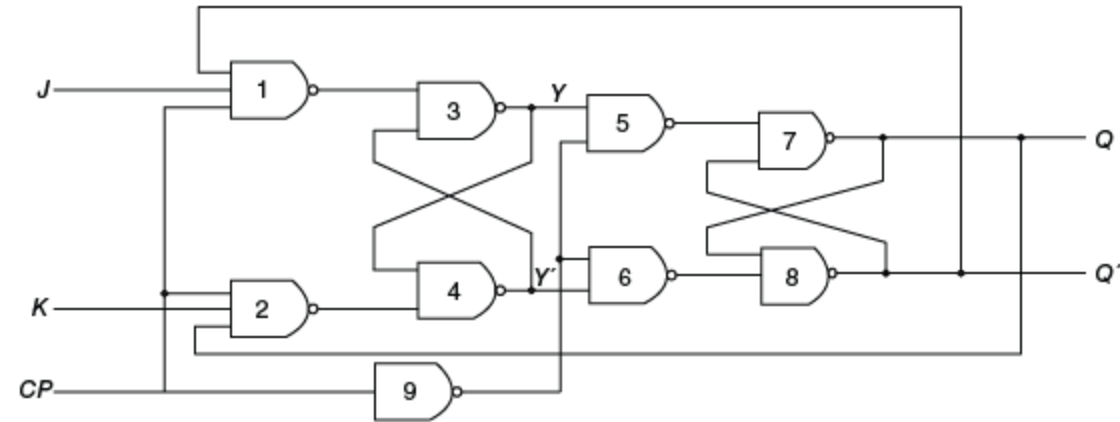- Gates 1 to 4: Master FF.
 - 5 to 8: Slave FF



Cascading of many Master-Slave FFs

- When pulse is 1 all the masters (internal to the FF) are enabled
 - O/p of the FFs are not affected.
- After the clock returns to 0.
 - Slaves are enabled.
 - O/ps of some of the FFs are changed.
 - None of the masters are affected by these changes.

Edge-Triggered Flip-Flop


- Output transitions occur at a specific level of the clock pulse
 - When the pulse input level exceeds this threshold level, i/ps are locked out.
 - Could be positive or negative edge triggered.

Design of Counters

- Counters: Sequential circuits which undergo **prescribed sequence of states** upon application of **i/p pulse**.
- I/p pulse: Called **count pulse**.
 - clock or from an external source.
 - Prescribed time or random.
- Sequence: binary (simplest and straightforward) or any other
- Used in all equipment with digital logic.
 - Number of occurrences.
 - Timing sequences to control operations.

Binary Counters

 - Simplest and straight forward.
- n-bit counter: **n FFs** and count from **0 to 2^n-1** .



- FF count **repeats**. Goes to 000 after 111.
- i/p and o/p values not shown.
- Clocked sequential circuits: State transitions during clock pulses. **Not shown** explicitly.
- Only i/p: **Count pulse**.
- O/ps: Specified by the **present states** of FFs.
- Next state
 - **Depends** only on the **present state**.
 - Transitions during clock pulses.
 - **Completely specified** by the count sequence.

Excitation Table for 3-bit counter

Table 6-12 Excitation table for a 3-bit binary counter

Count sequence			Flip-flop inputs		
A_2	A_1	A_0	TA_2	TA_1	TA_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	1	1	1

- **Next number** represents the **next state**.
- Count sequence:
Provides all information to design the circuit.
- Follows the **same procedure**.
- Excitation obtained **directly** from the count sequence.
- **Binary counters** most **effectively constructed** by T FFs.
- **Last row** compared with the first count **000**, its **next state**.

Memory Unit

- Operation register:
 - capable of **storing binary information** in its flip-flops
 - has **combinational gates** for **data-processing** tasks.
- Storage register:
 - **temporary storage** of binary information.
- *Memory Unit*: Collection of **storage registers** together with the **associated circuits** needed to **transfer** information in and out of the registers.
- *Memory registers*: **Storage registers** in a memory unit.
- **Most** of the **registers** in a digital computer are **memory registers**.
- Comparatively **few operational registers** are found in the processor unit.
- When data processing takes place:
 - **Information** from **selected registers** in memory unit is first **transferred** to **operational registers** in the processor unit.
 - **Intermediate** and **final** results obtained in the operational registers are **transferred back** to **selected memory registers**.


Basic properties of binary cells of Registers

- **Reliable two-state** property for binary representation.
- **Small** in size.
- **Cost per bit** of storage should be as **low** as possible.
- The **time of access** to a memory register should be **reasonably fast**.
- Examples of memory unit components
 - magnetic cores, semiconductor ICs, and magnetic surfaces on tapes, drums, or disks.

Memory Word


- *Words*: Memory unit stores binary information in **groups**.
- Each **word stored** in a **memory register**.
- Word is an **entity of n bits** that moves in and out of storage as a unit.
- A memory word may represent
 - an **operand**, an **instruction**, a group of **alphanumeric characters**, or any **binary-coded information**.

Block Diagram

 

- communication between a memory unit and its environment is achieved through
 - **two control signals**
 - **two external registers.**
 - The control signals specify the direction of transfer required whether
 - a word is to be stored in a memory register (**Write**)
 - whether a word previously stored is to be transferred out of a memory register. (**Read**)
-
- **Memory Address Register (MAR):** specifies the particular memory register chosen.
 - **Memory Buffer Register (MBR):** specifies the particular bit configuration of the word.

Block Diagram

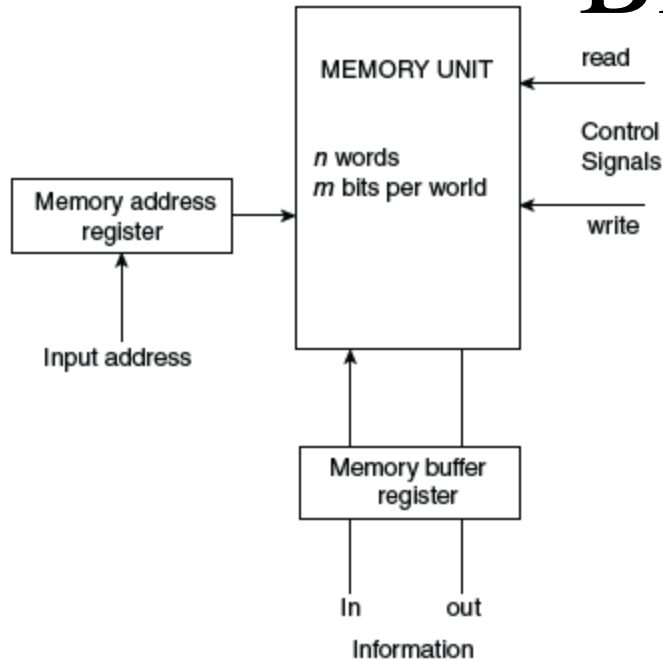


- Memory Address Register (MAR)
 - Specifies the **memory word selected**.
- Each word in memory
 - assigned a number **identification** starting from 0 to maximum number of words
- *Address of a word:*
 - transferred to MAR for communication.

- Internal circuits of the memory unit
 - accept this address from the register
 - open the paths needed to select the word called.
- An address register with n bits: specify up to 2^n memory words.

Computer memory units can range from 1024 words (**10 bit-MAR**) , to 1,048,576 (**20 bit- MAR**) = 2^{20} words,

Block Diagram

 


- Read:
 - internal control **sends** word from a memory register into the MBR.

- Memory Buffer Register (MBR)
 - **information transfer** to and from registers in memory and external environment
 - **Write**
 - internal control interprets: the **contents of the MBR** to be stored in a memory register.
- Contents of MAR specify particular memory register **referenced** for writing or reading


1024 words with eight bits per word.

- In MAR, we need an address of 10 bits ($2^{10} = 1024$)
- Hence 10 no. of FFs are required
- Similarly, MBR will have 8 no. of FFs
- Memory unit will have 1024 no. of Registers assigned with address 0 to 1023.

 Example: Initial conditions in the three registers




Read operation

 

- The **sequence of operations** needed to communicate with memory unit for transferring a word out to the MBR is:
- 1. **Transfer** the **address bits** of the selected word into **MAR**.
- 2. Activate the *read* control input.
- The binary information stored in memory register 42 is transferred into MBR.

Write Operation

 


- The **sequence of operations** needed to store a new word into memory is:
- 1. Transfer the **address bits** of the selected word into **MAR**.
- 2. Transfer the **data bits** of the word into **MBR**.
- 3. Activate the *write* control input.

Types of memory


- Using **Semiconductor IC**:
 - **Non destructive** Read.
 - **Retain** their information after Read.
 - **No loss** of information.
- Magnetic core:
 - **Destructive** Read-out.
 - **Losses** the stored information during Read.
 - must provide **additional control** functions **to restore** the word into the memory register

Read operation in Magnetic core memory

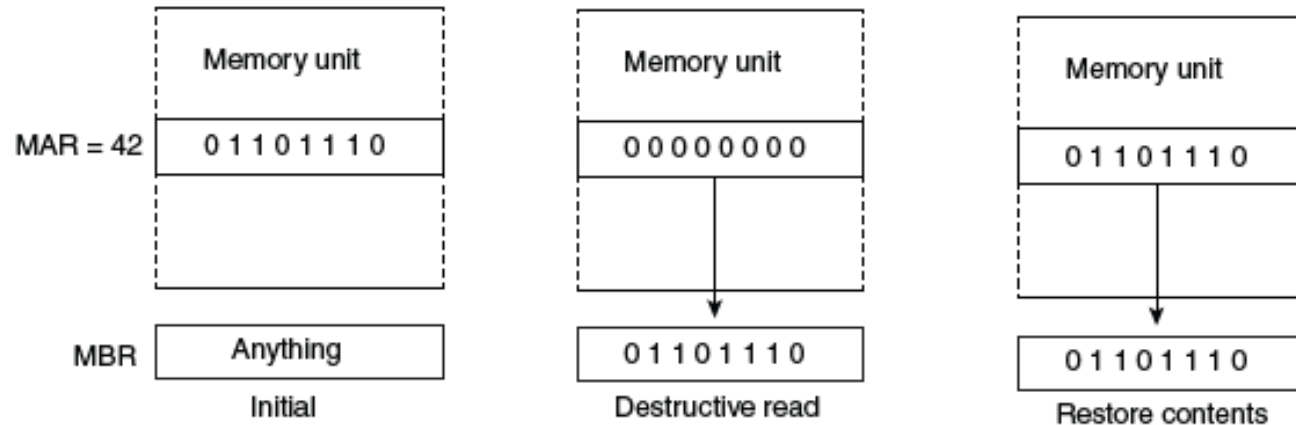



- During Restore **contents** of **MAR** and **MBR** must be **unchanged**.

Write operation in Magnetic core memory

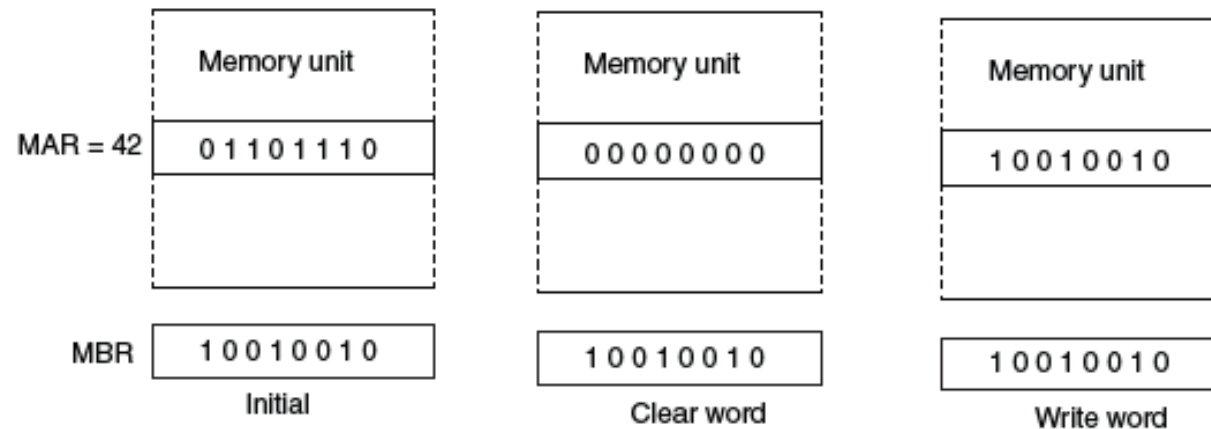


- **MAR must not change** during operation
 - To **ensure** that the **same selected word** cleared receives **information**.
- Magnetic-core memory requires **2 half-cycles** for reading or writing.
- **Time** to go through **both cycles**: **Memory-cycle** time.

Integrated Circuits memory (RAM)

  


- **Binary storage cell:** Basic building block of memory unit.
- **Must be very small**
 - To pack as many cells as possible.
- **3 i/ps and 1 o/p.**
- **Select i/p:** Enables cell for reading or writing.
- **Read/write:**
 - 1 for Read.
 - 0 for Write.
- **FF**
 - operates w/o clock pulses.
 - **Store** information bit

Integrated Circuits memory unit (RAM)

 


- **4 words of 3-bit each.**
- BC: Binary cell
- 2 address i/ps: to **2-to4 line decoder.**
- **Decoder** enabled by:
 - Memory enable i/p.
 - 0: no memory word selected.
 - 1: one of the 4 selected (address lines).

Integrated Circuits memory unit (RAM)

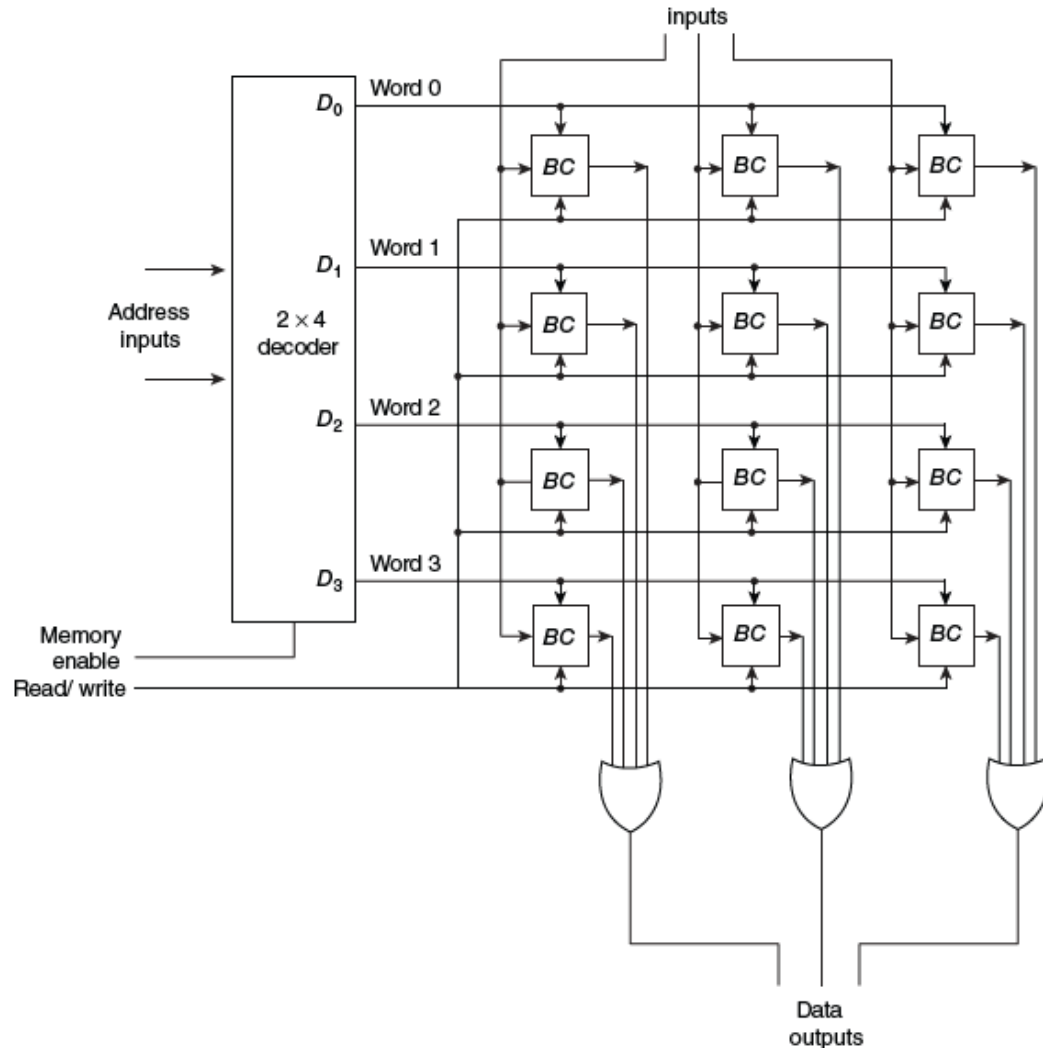

- Read/write:
 - 1:
 - Bits of selected word go through **3 OR gates** to o/p.
 - **Non-selected cells** produce **0's** at the i/ps of OR.

Integrated Circuits memory unit (RAM)

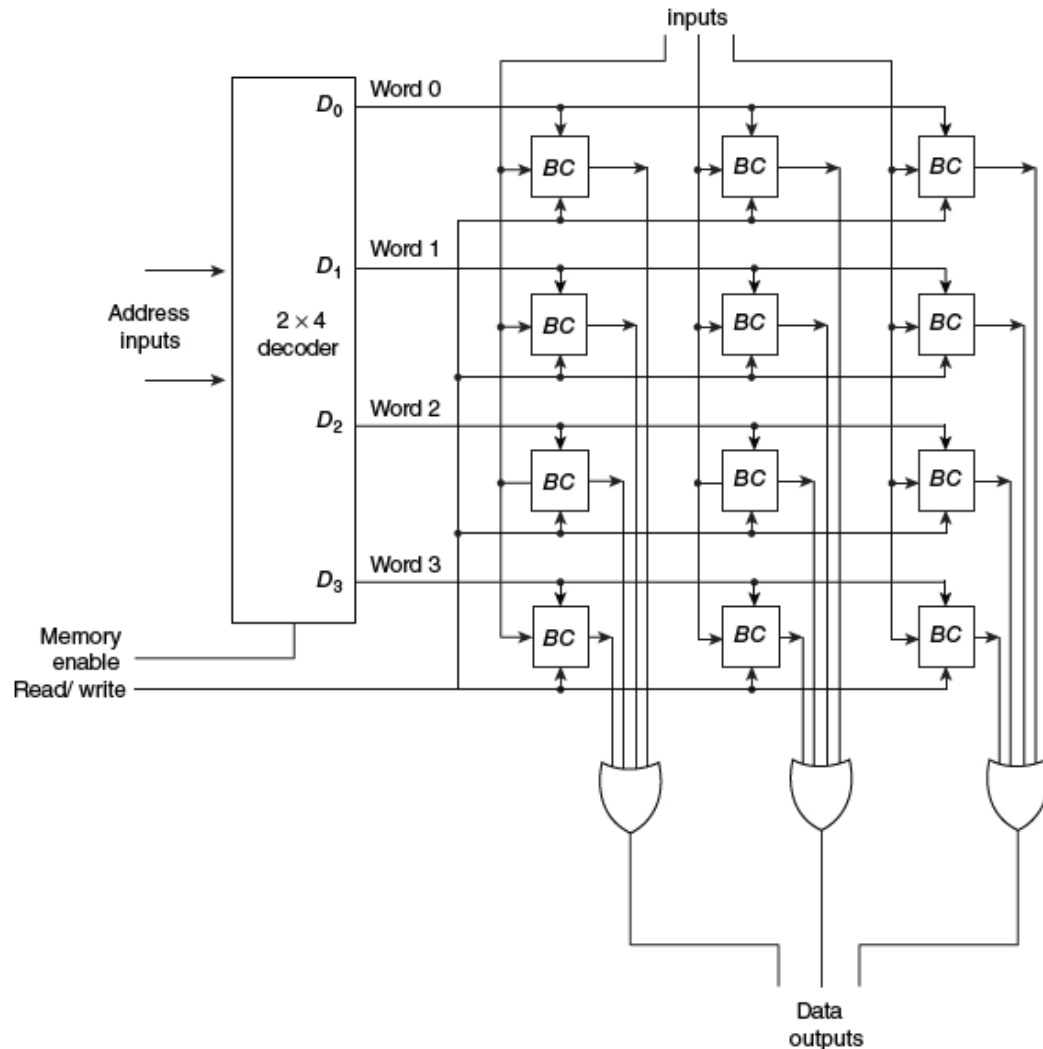


- Read/write:
 - 0:
 - Information in **i/p lines** transferred into BCs of selected word.
 - **Non-selected** BCs in other words **disabled** by their **selection i/ps** and their values are unchanged.
- With memory-enable=0
 - Contents of all cells in memory unchanged (regardless of read/write)

Magnetic core memory


- Magnetic core: Doughnut-shaped toroid.
- A **FF** requires **one physical quantity** for operation.
- Magnetic core: Uses **3** physical quantities.
 - Current, Magnetic flux and voltage
- **Excitation: By current pulse**
- Binary information represented by the **direction of magnetic flux** within core.
- O/p extracted as **voltage pulse**.

Magnetic core memory

 

- **Hysteresis loop, square loop:** With **zero current**, a flux either
 - **positive** (counter clockwise)
 - **Negative** (clockwise)**remains** in the magnetized core.
- **Current pulse** in the winding can **shift the direction** of magnetization.
- **Path flux follows with current pulse** indicated by arrows in **hysteresis loop**.


Magnetic core memory (Reading)

 

- **Reading:** Flux cannot be detected unless it is **changing**.
- Flux change wrt. time **induces** a **voltage** in wire that links the core.


- Read out: A **current** in the **negative** direction is applied
 - 1 state:
 - Current **reverses** the **direction** of magnetization.
 - **Resulting flux change** produces a **voltage pulse** in sense wire.
 - 0 state:
 - Core **magnetization not changed**.
 - Very **slight disturbance** of magnetic flux. (**small** o/p voltage in sense wire.)

Magnetic core memory unit

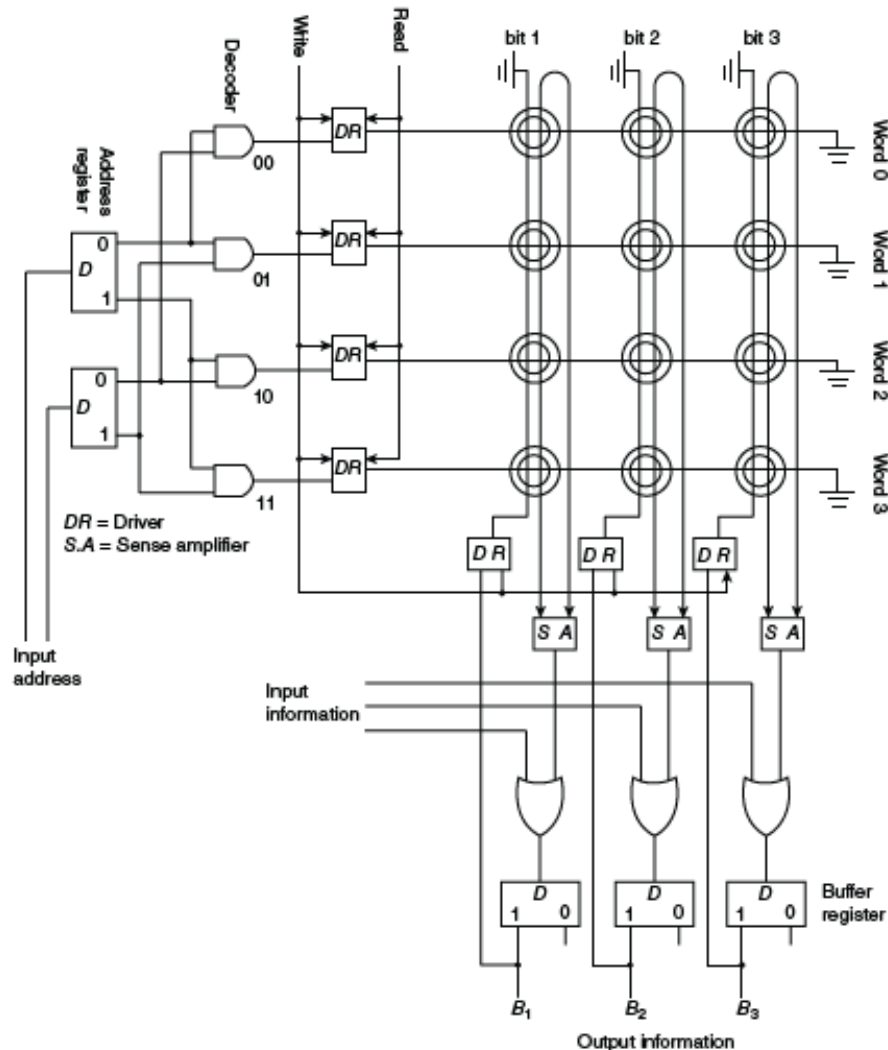


- **4 words with 3-bits each.**
- **Binary cell: Magnetic core with its wires.**
- **Excitation of core:**
 - **Current** pulse generated in driver (**DR**)
- **O/p: goes through a Sense Amplifier (SA)**
 - **Set** corresponding **FFs** in buffer register.

Magnetic core memory unit

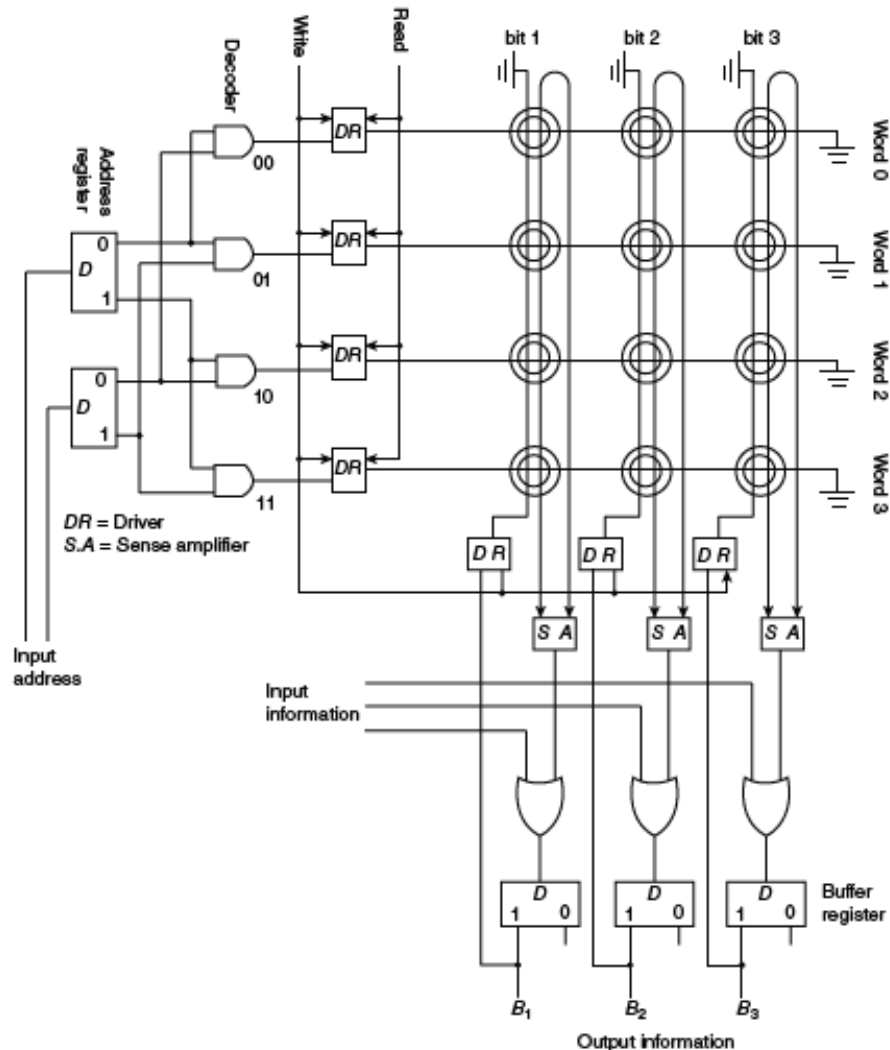


- **3 wires link each core:**
 - **Word wire:** Excited by word driver and goes through **three cores of a word**.
 - **Bit wire:** Excited by bit driver and goes through **four cores in same bit position**.
 - **Sense wire:** links the same cores as the bit wires.
 - Applied to SA
- **Sense Amplifier (SA):**
 - **Shapes** voltage pulse when **1 is read**.
 - **Rejects** small disturbance when **0 is read**.

Magnetic core memory unit (Read)

 

- **Word driver** pulse applied to the cores of the words selected by decoder.
- **Read current**
 - is in **negative** direction.
 - **all cores** of selected core go to '0' state.
- Cores with **1**
 - **Switch** their **flux**
 - **Induce** a **voltage** into their sense wire.
 - Voltage pulse is **amplified** in **SA**
 - **Sets** the corresponding **FF** in buffer register.
- Cores with **0**: **Flux** is **not changed**.

Magnetic core memory unit (Write)

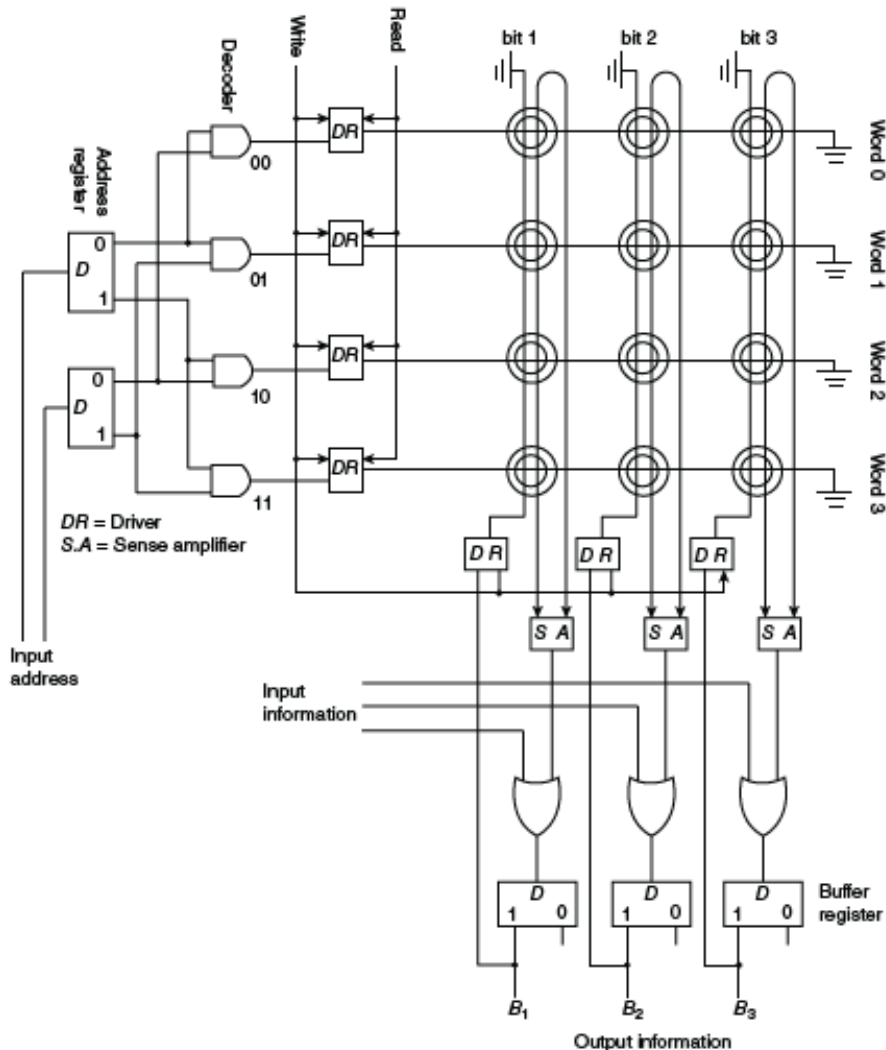

- **Buffer register** holds the information to be stored in the word specified by address register.
- **Assume** that all cores in the selected word are **initially cleared**.
- For **writing 1**: A current pulse is generated **simultaneously** in
 - **Word driver** selected by decoder
 - **Bit driver** with corresponding buffer register **FF=1**.
- Both current in **positive direction**.
 - Magnitude is only **half needed** to switch the flux to 1 state.
- Direction of magnetization **does not change** if it receives **only one half** current.

Complete picture

- Read:
 - Selected word is **destroyed**.
 - Should be followed by **restoration**
 - Restore: **equivalent** to **write** operation. (Buffer register to selected word)
- Write:
 - Cores are **initially cleared**.
 - **Equivalent** to **Read** operation. (destruction of stored information)
 - But **prevents the Read information** from **reaching buffer register** by **inhibiting SA**.
- Restore and clear cycles **initiated** by memory **internal control** .
 - Outside world memory unit appears nondestructive.

Review

- Flip-Flops
- Triggering of Flip-Flops
- Analysis of clocked sequential circuits
- State reduction and Assignment
- Flip-Flop Excitation Tables
- Conversion of one FF to another
- Design Procedure
- Design of counters
- Shift registers