

In this topic, We'll learn

- Adders
- Subtractors
- Code convertors
- Analysis procedure

Introduction

- Logical circuits

1. Combinational circuits


- Made of logical gates
- Outputs at any time are directly determined by the present combination of i/ps. (do not depend on previous i/ps)
- Performs information processing operation specified by a set of Boolean functions.

2. Sequential circuits

- Made of logical gates and memory elements (binary cells).
- Outputs at any time are determined by the present combination of i/ps and the state of the memory elements.
- State of memory elements is a function of previous i/ps.

Combinational circuit

 - n i/p variables
 - 2^n combinations of binary i/p values possible.
 - for each i/p combination there is only and one o/p combination possible.
- A combinational circuit can be represented by
 - m Boolean functions, one for each o/p variable.
 - each o/p function is expressed in terms of n i/p variables.



- Each i/p variable to a combinational circuit may have
 - One wire (either normal or complement form)
 - or two wires (both normal and complement form)
- Flip Flops (binary cells for storage) have o/ps in both forms.

Design Procedure

1. The problem is **stated**.
2. The number of available **input** variables and **required output** variables is **determined**.
3. The input and output variables are **assigned** letter **symbols**.
4. The **truth table** that defines the required relationships between inputs and outputs is derived.
5. The **simplified Boolean function** for each output is **obtained**.
6. The **logic diagram** is drawn.

Simplified expressions


- Application specific.
- Depends on constraints such as
 - Minimum number of gates.
 - Minimum number of i/ps to a gate.
 - Minimum propagation time of the signal through the circuit.
 - Minimum number of interconnections.
 - Limitations on the driving capabilities of the gate.

Adders

- Digital computers perform a variety of information-processing tasks.
 - Includes various arithmetic operations.
- Most basic arithmetic operation
 - Addition of two bits
- Half-adder: Combinational circuit that performs addition of two bits.
- Full-adder: Performs addition of three bits.
 - Two half-adders can be employed to implement a full-adder.

Half-adder


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


$$S = x'y + xy'$$

$$C = xy$$


Various implementations of half-adder

 


(a) $S = xy' + x'y$
 $C = xy$

 


(b) $S = (x + y) (x' + y')$
 $C = xy$

 

(c) $S = (C + x'y')'$
 $C = xy$

 

 (d) $S = (x + y) (x' + y')$
 $C = (x' + y')'$



(e) $S = x \oplus y$
 $C = xy$


Full-adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

Implementation of Full Adder Circuit

 

Implementation of Full-adder with 2 HA.

 

$$\begin{aligned} S &= z \oplus (x \oplus y) \\ &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= xy'z' + x'yz' + xyz + x'y'z \end{aligned}$$


$$C = z(xy' + x'y) + xy = xy'z + x'yz + xy$$

Subtractors

- If the minuend (1^{st}) bit is smaller than the subtrahend (2^{nd}) bit
 - A **1** is borrowed from the next significant position.
 - Conveyed to next pair of higher bits by Borrow bit (B).

Half-Subtractor

x	y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

 

$$D = x'y + xy'$$

$$B = x'y$$

Full-subtractor


- Performs a subtraction between two bits
 - Takes in to account a 1 may have been borrowed by a lower significant stage.
 - 3 i/ps and 2 o/ps.

Full-adder to Full-subtractor

x	y	z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = x'y'z + x'yz' + xy'z' + xyz$$

$$B = x'y + x'z + yz$$

 





Code Conversion

- A large variety of codes are available for the same discrete elements.
 - Different codes are used by different digital systems.
- Code conversion is used when connecting two such digital systems to make them compatible.
- To convert code A to code B
 - i/p is A.
 - o/p generated corresponding bit combination of code B.
 - Combinational circuits using logical gates is used for this transformation.

BCD to excess-3 code

Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

    


$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$$

$$= B'(C + D) + B(C + D)'$$


$$w = A + BC + BD = A + B(C + D)$$

 

Analysis Procedure

- Reverse problem
 - Starts with a logic diagram
 - Culminates with a Boolean expression or truth table.
- Methods used
 - Derivation of the Boolean Function by Algebraic Manipulation
 - Derivation of the Truth Table
 - Block Diagram Transformation

 Derivation of the Boolean Function by Algebraic Manipulation



$$T_1 = (CD)' = C' + D'$$

$$T_2 = (BC')' = B' + C$$

$$\begin{aligned} T_3 &= (B'T_1)' = (B'C' + B'D')' \\ &= (B + C)(B + D) = B + CD \end{aligned}$$

$$T_4 = (AT_3)' = [A(B + CD)]'$$


$$\begin{aligned} F &= (T_2 T_4)' = \{(BC')'[A(B + CD)]'\}' \\ &= BC' + A(B + CD) \end{aligned}$$

Derivation of the Truth Table



TABLE 4-3
Truth Table for the Circuit of Figure 4-14

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>T</i> ₁	<i>T</i> ₂	<i>T</i> ₃	<i>T</i> ₄	<i>F</i>
0	0	0	0	1	1	0	1	0
0	0	0	1	1	1	0	1	0
0	0	1	0	1	1	0	1	0
0	0	1	1	0	1	1	1	0
0	1	0	0	1	0	1	1	1
0	1	0	1	1	0	1	1	1
0	1	1	0	1	1	1	1	0
0	1	1	1	0	1	1	1	0
1	0	0	0	1	1	0	1	0
1	0	0	1	1	1	0	1	0
1	0	1	0	1	1	0	1	0
1	0	1	1	0	1	1	0	1
1	1	0	0	1	0	1	0	1
1	1	0	1	1	0	1	0	1
1	1	1	0	1	1	1	0	1
1	1	1	1	0	1	1	0	1

Block Diagram Transformation

 

$$F = AB + BC' + ACD$$

  

Review

- Solve unsolved problems for the topics covered.