

Chapter 2

Boolean Algebra

Morris Mano, “Digital Logic and Computer Design.” (Pearson India, 2017)

In this topic, we'll learn

- Primitive logic elements used in digital systems.
- Mathematical methods for designing circuits.
- Cost effective design.
- Optimization techniques.

Binary Logic

- Deals with
 - variables that take on two discrete values
 - operations that assume logical meaning.
- Two values the variables take may be called by different names. (e.g., *true* and *false*, *yes* and *no*, etc.)
- Convenient to use bits and assign the values of 1 and 0.
- Used to describe mathematically the manipulation and processing of binary information.
- Suited for the analysis and design of digital systems.

Definition of Binary Logic

- Consists of binary variables (A, B, C, y, z etc.,) and logical operations.
- Each variable can have two and only two distinct possible values: 0 and 1.
- Basic logical operations: AND, OR and NOT.

AND operation

- Represented by ‘.’ or absence of an operator.

$$X.Y=Z \text{ or } XY=Z.$$

- Can be considered as two switches connected in series.

AND		
X	Y	Z = X · Y
0	0	0
0	1	0
1	0	0
1	1	1

OR operation

- Represented by '+’.
- Can be considered as two switches connected in parallel.

OR		
X	Y	Z = X + Y
0	0	0
0	1	1
1	0	1
1	1	1


NOT Operation

- Represented by a ' or by a bar.


NOT	
X	Z = \bar{X}
0	1
1	0

Switching Circuits and Binary Signals

 - Manual switches A and B represent two binary variables.
 - equal to 0 when the switch is open and 1 when the switch is closed.
- Lamp L represent a third binary variable
 - equal to 1 when the light is on and 0 when off.
- Electronic digital circuits: Switching circuits
 - Active element such as transistor acts as **closed** switch **when conducting** and **open** switch **other wise**.




(a) Switches in series – logic AND

 

 (b) Switches in parallel – Logic OR

Logic gates

- Electronic digital circuits are also called Logic gates.
 - with the proper input, they establish logical manipulation paths.



Gates are implemented using transistors.
Signals are voltages or currents.

Symbols for digital logic circuits


- These circuits are called *gates*.
- Four different names are used:
 - digital circuits, switching circuits, logic circuits, and gates
- We prefer to call them gates.
- Not gate is also called an inverter circuit.




(a) Two-input AND gate




(b) Two-input OR gate

 

(c) NOT gate or inverter

 


(d) Three-input AND gate

 


(e) Four-input OR gate

Input-output signals for gates

 

Boolean Algebra

 

- Mathematical system of binary logic is better known as Boolean, or switching, algebra.
 - conveniently used to describe the operation of complex networks of digital circuits.
- Designers of digital systems use Boolean algebra
 - to transform circuit diagrams to algebraic expressions and vice versa.
- Mathematical notion used is Boolean Algebra.
- George Boole, 1854.

History

- In 1854 George Boole introduced a systematic treatment of logic: Boolean Algebra
- In 1938 C. E. Shannon (2) introduced a two-valued Boolean algebra called *switching algebra*,
 - he demonstrated that the properties of bistable electrical switching circuits can be represented by this algebra.
- Postulates formulated by E. V. Huntington in 1904 are used for formal definition of Boolean Algebra.

Definition of Boolean Algebra

- An algebraic structure defined on a set of elements B together with two binary operators $+$ and \bullet provided the following (Huntington) postulates are satisfied.

1.

(a) Closure with respect to the operator $+$.

(b) Closure with respect to the operator \bullet .

2.

(a) An identity element with respect to $+$, designated by 0:

$$x + 0 = 0 + x = x.$$

(b) An identity element with respect to \bullet , designated by 1:

$$x \bullet 1 = 1 \bullet x = x.$$

Definition of Boolean Algebra (continued)

3.

(a) Commutative with respect to $+$: $x + y = y + x$.

(b) Commutative with respect to \bullet : $x \bullet y = y \bullet x$.

4.

(a) \bullet is distributive over $+$: $x \bullet (y + z) = (x \bullet y) + (x \bullet z)$.

(b) $+$ is distributive over \bullet : $x + (y \bullet z) = (x + y) \bullet (x + z)$.

5. For every element $x \in B$, there exists an element $x' \in B$ (called the complement of x) such

that: (a) $x + x' = 1$ and (b) $x \bullet x' = 0$.

6. There exists at least two elements $x, y \in B$ such that $x \neq y$.

Boolean vs ordinary algebra

- Huntington postulates do not include the associative law. (this is true).
- The distributive law of $+$ over \bullet , i.e., $x + (y \bullet z) = (x + y) \bullet (x + z)$, is valid for Boolean algebra, but not for ordinary algebra.
- Boolean algebra does not have additive or multiplicative inverses; therefore, there are no subtraction or division operations.
- *complement* is not available in ordinary algebra.
- Ordinary algebra deals with the real numbers, which constitute an infinite set of elements. B, for our purpose, is defined as a set with only two elements, 0 and 1 in Boolean algebra.
- **Our interest here is with the application of Boolean algebra to gate-type circuits.**

Two-Valued Boolean Algebra

- Defined on a set of two elements, $B = \{0, 1\}$ with
 - rules for the two binary operators $+$ and \cdot as shown below

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

- Closure, Identity and commutative properties are easily verified from the table.

Continued...

- *distribute* law: $x \bullet (y + z) = (x \bullet y) + (x \bullet z)$

x	y	z		$y + z$	$x \bullet (y + z)$		$x \bullet y$	$x \bullet z$	$(x \bullet y) + (x \bullet z)$
-----	-----	-----	--	---------	---------------------	--	---------------	---------------	---------------------------------

Continued...

- *distribute* law $x \bullet (y + z) = (x \bullet y) + (x \bullet z)$

$x \ y \ z$	$y + z$	$x \bullet (y + z)$	$x \bullet y$	$x \bullet z$	$(x \bullet y) + (x \bullet z)$
0 0 0	0	0	0	0	0
0 0 1	1	0	0	0	0
0 1 0	1	0	0	0	0
0 1 1	1	0	0	0	0
1 0 0	0	0	0	0	0
1 0 1	1	1	0	1	1
1 1 0	1	1	1	0	1
1 1 1	1	1	1	1	1

continued

- Property 5
 - $x + x' = 1$
 - $x \cdot x' = 0$
- Postulate 6 is satisfied because the two-valued Boolean algebra has two distinct elements
 - 1 and 0 with $1 \neq 0$.
- Two binary operators with operation rules equivalent to the AND and OR operations.
- Complement operator equivalent to the NOT operation.
- Equivalent to the binary logic presented earlier.

Postulates and theorems of Boolean algebra

Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x' y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

- *Duality principle: Arranged as 2 columns*

Operator Precedence

- (1) parentheses, (2) NOT, (3) AND, and (4) OR.
- Eg: $(A + B)' = A' \cdot B'$.

Using basic Boolean theorem prove:

1. $(x + y)(x + z) = x + yz$

2. $xy + xz + yz' = xz + yz'$

Sol. 1: $(x + y)(x + z)$

$xx + xz + xy + yz$

$x + xz + xy + yz$

$x(1 + z) + xy + yz$

$x + xy + yz$

$x(1 + y) + yz$

$x + yz$

Sol. 2: $xy + xz + yz'$

$xy(z + z') + xz + yz'$



$xyz + xyz' + xz + yz'$

$xz(1 + y) + yz'(1 + x)$

$xz + yz'$

Venn Diagram

  - Aids in the visualization of Boolean relations between variables.



$$X = X + XY$$

Boolean Functions

- A Boolean function is an expression formed with
 - binary variables
 - the two binary operators OR and AND,
 - the unary operator NOT,
 - parentheses, and equal sign
- For a given value of the variables, the function can be either 0 or 1.

e.g.: $F_1 = xyz'$

Boolean function represented as an **algebraic expression**.


Truth Table for Boolean function $F_1 = xyz'$

x	y	z	F_1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0


Truth Table for Boolean function $F_1 = xyz'$,
 $F_2 = x + y' z$, $F_3 = x' y' z + x' yz + xy'$, and
 $F_4 = xy' + x' z$

x	y	z	F_1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

 
Implementation of Boolean function with gates



(a) Two-input AND gate

 


(b) Two-input OR gate

 

 
(c) NOT gate or inverter

- $F_1 = xyz'$


Implementation of Boolean function with gates



(a) Two-input AND gate

 


(b) Two-input OR gate

 


(c) NOT gate or inverter


- $F_1 = xyz'$

 

 
Implementation of Boolean function with gates



(a) Two-input AND gate

 


(b) Two-input OR gate

 

 
(c) NOT gate or inverter

- $F_2 = x + y' z$
- $F_3 = x' y' z + x' y z + x y'$
- $F_4 = x y' + x' z$


Implementation of Boolean function with gates



(a) Two-input AND gate


 


(b) Two-input OR gate

 

  (c) NOT gate or inverter

- $F_2 = x + y' z$
- $F_3 = x' y' z + x' y z + x y'$
- $F_4 = x y' + x' z$



How to manipulate Boolean functions to obtain equal and simpler expressions?

Best form of Boolean Function

- Depends on the particular application.
- Here we consider criterion of equipment minimization.

Algebraic Manipulation

- *Literal* is a primed or unprimed variable.
- While implementing
 - each literal in the function designates an input to a gate.
 - each term is implemented with a gate.
- Minimization of the number of literals and the number of terms results in a circuit with less equipment.
- Here we will emphasize on **literal minimization**.
- Algebraic manipulation
 - Unfortunately, there are **no specific rules** to follow that will guarantee the final answer.
 - employ the postulates, the basic theorems, and other manipulation methods

Simplify the following equations

- $x + x' y$
- $x (x' + y)$
- $x' y' z + x' yz + xy'$
- $xy + x' z + yz$
- $(x + y) (x' + z) (y + z)$

Simplify the following equations

- $x + x' y = x + y$
- $x (x' + y) = x y$
- $x' y' z + x' y z + x y' = x' z + x y'$
- $x y + x' z + y z = x y + x' z$
- $(x + y) (x' + z) (y + z) = (x + y) (x' + z)$

Complement of a Function

- Complement of a function may be derived algebraically through De Morgan's theorem.
- De Morgan's theorems can be extended to three or more variables.

Complement of a Function

- Complement of a function may be derived algebraically through De Morgan's theorem.
- De Morgan's theorems can be extended to three or more variables.

$$(A + B + C + D + \dots + F)' = A'B'C'D' \dots F'$$

$$(ABCD \dots F)' = A' + B' + C' + D' + \dots + F'$$

- Complement of a function is obtained by interchanging AND and OR operators and complementing each literal.

Find the complement of functions using
De Morgan's theorem:

- $F_1 = x' yz' + x' y' z$
- $F_2 = x(y'z' + yz)$

Find the complement of functions using duals:

1. *Find the dual of the function.*
2. *Complement the literal*

- $F_1 = x' y z' + x' y' z$

1. $(x' + y + z').(x' + y' + z)$

2. $(x + y' + z).(x + y + z')$

- $F_2 = x(y' z' + y z)$

- 1.

- 2.

Canonical Forms

- A binary variable may appear in
 - Normal form (x)
 - Complimentary form (x')
- Hence for two variables x and y there are four possibilities for AND operation
 - $x'y'$, $x'y$, xy' , and xy
 - Each of these 4 terms is called a **min-term** or **standard product**.
 - n variables : 2^n minterms (binary numbers from 0 to $2^n - 1$).
 - Each minterm: AND term of n variables which is primed if the corresponding bit is 0. (Symbol m_j , where j is the decimal equivalent of binary number)

Minterms

Table 2-3 Minterms and maxterms for three binary variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Canonical Forms (continued..)

- Similarly for an OR
 - n variables from 2^n terms called **maxterms** or **standard sums**.
 - each variable being unprimed if the corresponding bit is a 0 and primed if a 1. (Symbol: M_j)

Minterms and maxterms for three binary variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Minterms and Maxterms

Table 2-3 Minterms and maxterms for three binary variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Boolean function as sum of minterms

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

			Minterms	
x	y	z	Term	Designation
0	0	0	$x'y'z'$	m_0
0	0	1	$x'y'z$	m_1
0	1	0	$x'yz'$	m_2
0	1	1	$x'yz$	m_3
1	0	0	$xy'z'$	m_4
1	0	1	$xy'z$	m_5
1	1	0	xyz'	m_6
1	1	1	xyz	m_7

Maxterms directly from the truth table

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Any Boolean function can be expressed as a product of maxterms or sum of minterms.
- Boolean functions expressed as a sum of minterms or product of maxterms are said to be in *canonical form*.

Sum of Minterms

- Minterms whose sum defines the Boolean function are those that give the 1's of the function in a truth table.
- Conversion to sum of minterms:
 - If a term misses one or more variables, it is ANDed with an expression such as $x + x'$, where x is one of the missing variables.
- E.g.: Express the Boolean function $F = A + B'C$ in a sum of minterms.

Sum of Minterms

- Minterms whose sum defines the Boolean function are those that give the 1's of the function in a truth table.
- Conversion to sum of minterms:
 - If a term misses one or more variables, it is ANDed with an expression such as $x + x'$, where x is one of the missing variables.
- E.g.: Express the Boolean function $F = A + B'C$ in a sum of minterms.
- $F = m_1 + m_4 + m_5 + m_6 + m_7 = \Sigma (1, 4, 5, 6, 7)$

Product of Maxterms

1. Use distributive law to bring to a form of OR terms.
2. Missing variable x in each OR term is ORed with xx' .

E.g.: $F = xy + x'z$

Product of Maxterms

1. Use distributive law to bring to a form of OR terms.
2. Missing variable x in each OR term is ORed with xx' .

E.g.: $F = xy + x'z = M_0 M_2 M_4 M_5 = \Pi(0, 2, 4, 5)$

Table 2-3 Minterms and maxterms for three binary variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Conversion between canonical forms

- The complement of a function expressed as the sum of minterms equals the sum of minterms missing from the original function.
- $F(A,B, C) = \Sigma(1,4,5,6,7)$
- $F' (A,B, C) = \Sigma()$

Conversion between canonical forms

- The complement of a function expressed as the sum of minterms equals the sum of minterms missing from the original function.
- $F(A,B, C) = \Sigma(1,4,5,6,7)$
- $F' (A,B, C) = \Sigma(0,2,3)$
- Complement of F' by De Morgan's theorem gives F in another form

Table 2-3 Minterms and maxterms for three binary variables

x	y	z	Minterms		Maxterms	
			Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

Conversion between canonical forms

- The complement of a function expressed as the sum of minterms equals the sum of minterms missing from the original function.
- $F(A,B, C) = \Sigma(1,4,5,6,7)$
- $F' (A,B, C) = \Sigma(0,2,3)$
- Complement of F' by De Morgan's theorem gives F in another form
- $F = (m_0 + m_2 + m_3)' = m'_0 . m'_2 . m'_3 = M_0 M_2 M_3 = \Pi (0, 2, 3)$
- $m_j' = M_j$

General conversion procedure

- To convert from one canonical form to another
 - interchange the symbols Σ and Π
 - list those numbers missing from the original form.
- *Convert* $F(x, y, z) = \Pi (0, 2, 4, 5)$ to Sum of minterms form.
- $\Sigma (1,3,6,7)$

Standard Forms

- Two canonical forms of Boolean algebra are basic forms that one obtains from reading a function from the truth table.
 - seldom the ones with the least number of literals (should include by definition all variables)
- Standard form
 - function may contain one, two or any number of literal.
 - 2 types: the sum of products and product of sums.
 - $F_1 = y' + xy + x'yz'$: SOP
 - $F_2 = x(y' + z)(x' + y + z' + w)$: POS

Conversion from non-standard form to standard form

- $$\begin{aligned} F3 &= (AB + CD)(A'B' + C'D') \\ &= ABA'B' + ABC'D' + A'B'CD + CDC'D' \\ &= ABC'D' + A'B'CD \end{aligned}$$





Other Logic Operations

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
Operator																	
Symbol				/		/		\oplus	+	\downarrow	\odot		\subset		\supset	\uparrow	

Boolean expressions for the 16 functions of two variables

$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	x/y	Inhibition	x but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$x \odot y$	Equivalence*	x equals y
$F_{10} = y'$	y'	Complement	Not y
$F_{11} = x + y'$	$x \supset y$	Implication	If y then x
$F_{12} = x'$	x'	Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

Digital logic gates

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	

NAND



$$F = (xy)'$$

x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

NOR



$$F = (x + y)'$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR
(XOR)



$$F = xy' + x'y$$

$$= x \oplus y$$

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

Exclusive-NOR
or
equivalence



$$F = xy + x'y'$$

$$= x \odot y$$

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1


Extension to Multiple Inputs

- A gate can be extended to have multiple inputs if binary operation it represents is
 - commutative
 - and associative
 - AND and OR are commutative and associative.
 - gate inputs can be interchanged.
- What about NAND and NOR?


Extension to Multiple Inputs

- A gate can be extended to have multiple inputs if binary operation it represents is

 - commutative
- and associative
- AND and OR are commutative and associative.
- gate inputs can be interchanged.



 - What about NAND and NOR?
 - Commutative but not associative.




- To overcome this we define NAND and NOR as

$$x \downarrow y \downarrow z = (x + y + z)'$$


$$x \uparrow y \uparrow z = (xyz)'$$

Cascaded NAND

 

- Write the output



Cascaded NAND

 

- Correct parentheses should be used to signify the proper sequence.
- Sum of products can be implemented with NAND gates

Cascaded XOR and Equivalence

  - Both are commutative and associative.
 - can be extended to more than two inputs.



x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Construct AND/OR Gate using NOR/NAND Gate

